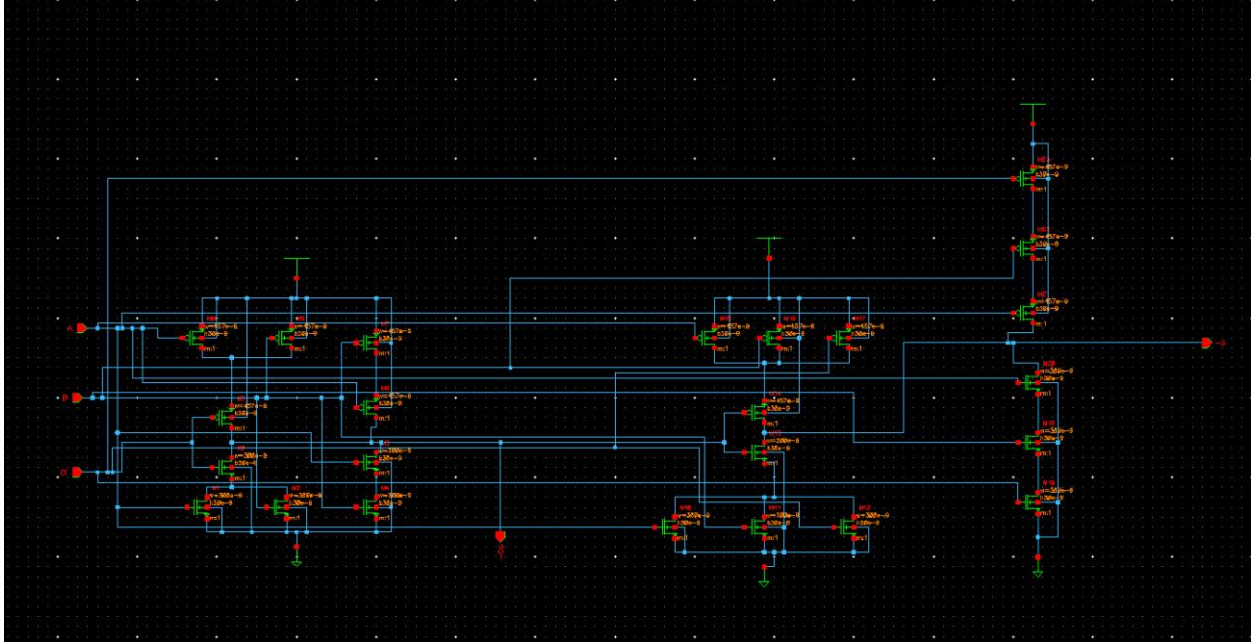


ASUID:-1233676836

EEE 591

LAB #04

1. Full adder schematic and sizing




Nmos:300nm

Pmos:457nm


a. Explain the sizing criteria used

Mirror Adder

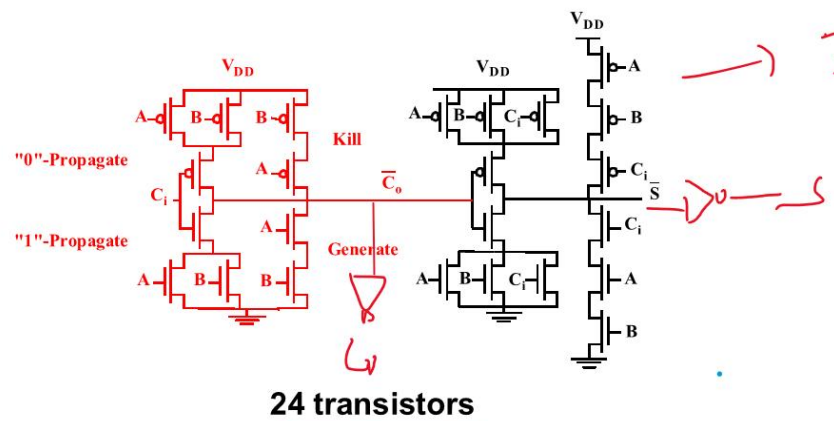

Name :- Tianyu Chen

ASUID:-1233676836

 


The minimum sized NMOS transistor you can use has $W_N = 300\text{nm}$; I choose the mirror adder because it is easier to size the pmos transistor; all the pull-up network and pull-down network are symmetric; so I can sweep the pmos transistor sizes and get the suitable sizes to let W_p to match the LH and HL delay.

b. Provide the sizes (W/L) of all your transistors

All the nmos transistors: 300nm ; All the pmos transistors: 457nm

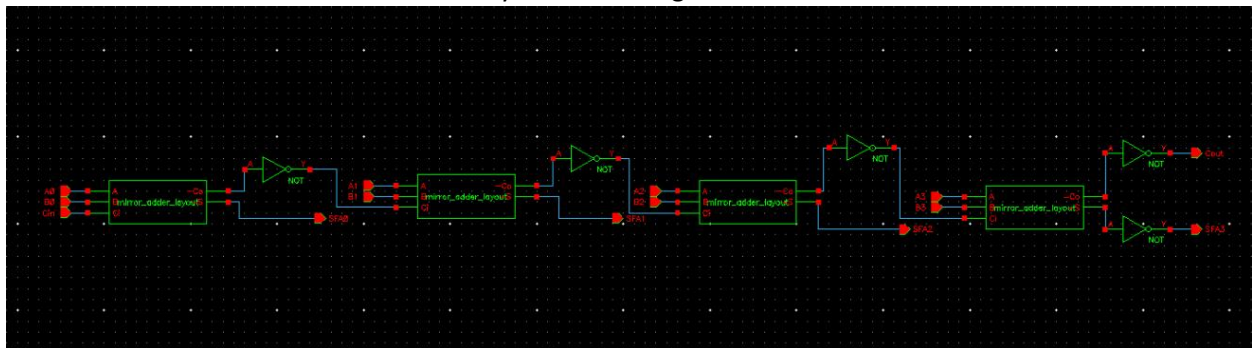c. Provide the schematic of your 4-bit design



d. Provide any scaling you choose to do for the 4-bit design and justification for the choice

I put the inverter outside the 1-bit adder design, and I just add the inverter to the Cout; I only have 5 inverters in my design. And it is easy to design and layout for the mirror_adder.

Name :- Tianyu Chen

ASUID:-1233676836


•**Simplicity:** The ripple-carry adder is easy to design and implement. It simply consists of a series of full adders (FA), each responsible for adding a bit from each operand along with a carry bit from the previous stage.

•**Low Hardware Cost:** Due to its simple design, the ripple-carry adder requires fewer components compared to other types of adders like carry-lookahead adders. It is cost-effective in terms of area and power consumption.

2. Simulation results


a. Include the worst case delay plots

Worst case delay = 231ps

 

b. Include the power consumption analysis results

Power=21.784uw

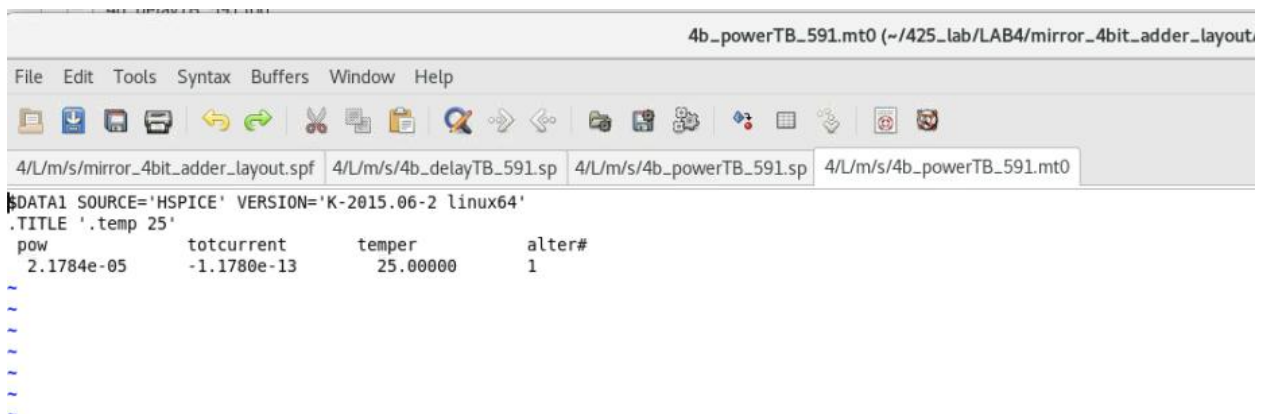


3. Include confirmation of


a. Layout & DRC Pass

Name :- Tianyu Chen

ASUID:-1233676836

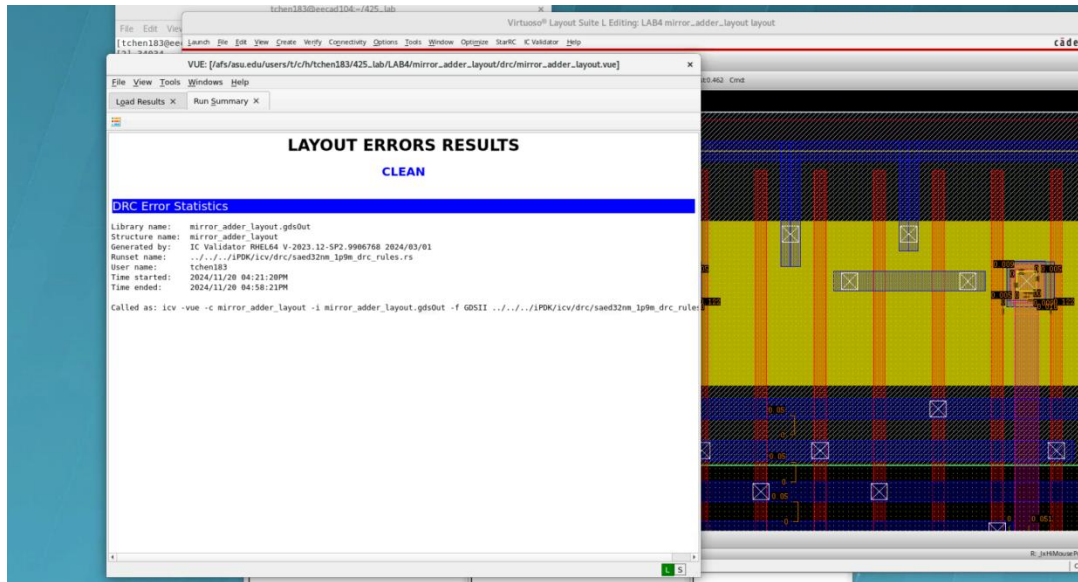

b. Layout & LVS Pass

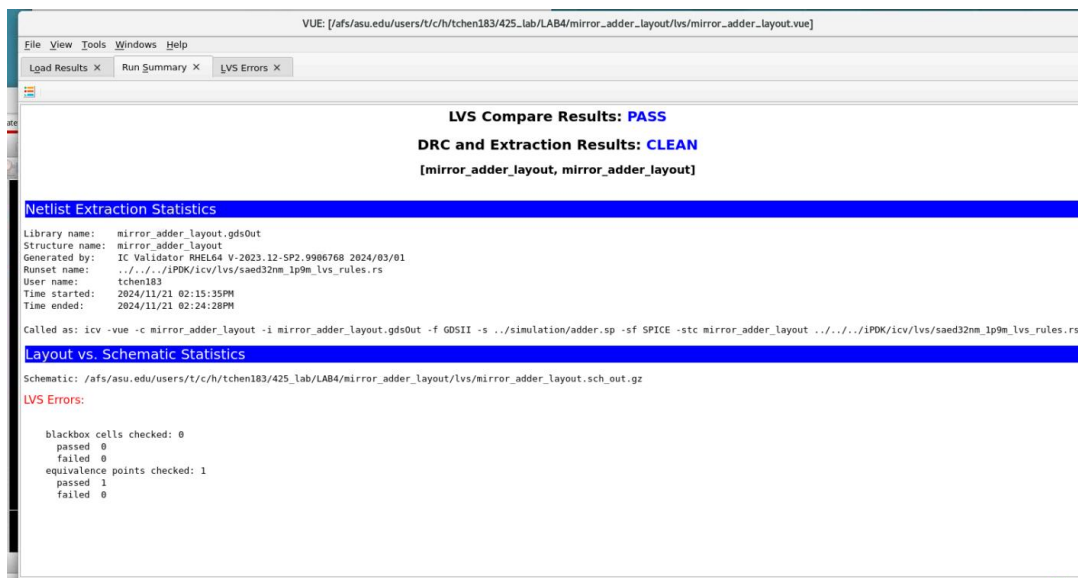

4. Report the total area of your layout

Name :- Tianyu Chen

ASUID:-1233676836



Width = 9.624um

Height = 1.7um

Area = width * height = 16.3608um²


- Report your overall score as outlined in the lab document

Score: The overall score for your design is calculated based on the following formula:

$$Score = \frac{400ps}{Delay} + \frac{100\mu W}{Power} + \frac{150\mu m^2}{Area}$$

Delay	231ps
Power	21.784uw
Area	16.3608um ²
Score	15.5

1-bit adder layout

 

Name :- Tianyu Chen

ASUID:-1233676836

4-bit adder layout

